

HW1

劉宗岳 108061532 電機系碩一

a. Truth table

X1	X2	X3	a	b	z
0	0	0	1	1	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	0	0	1

```
alumni [/u/cs/104/0413249] -zyliu- g++ 108061532.cpp
alumni [/u/cs/104/0413249] -zyliu- ./a.out
Truth table
x1 = 0 x2 = 0 x3 = 0 a = 1 b = 1 z = 0
x1 = 0 x2 = 0 x3 = 1 a = 1 b = 0 z = 0
x1 = 0 x2 = 1 x3 = 0 a = 1 b = 0 z = 0
x1 = 0 x2 = 1 x3 = 1 a = 1 b = 0 z = 0
x1 = 1 x2 = 0 x3 = 0 a = 1 b = 1 z = 0
x1 = 1 x2 = 0 x3 = 1 a = 1 b = 0 z = 0
x1 = 1 x2 = 1 x3 = 0 a = 0 b = 0 z = 1
x1 = 1 x2 = 1 x3 = 1 a = 0 b = 0 z = 1
```

b. Report the cardinalities of the ON-SET and the OFF-SET of the internal signals a, b, and primary output signal z, respectively

ANS:

ON SET cardinality of signal a = 6, signal b = 2, signal z = 2

OFF SET cardinality of signal a = 2, signal b = 6, signal z = 6

- c. Find out all input vectors that can excite signal a stuck-at-1 fault. List your results as a table and report their total number.

ANS:

input vector $(x_1, x_2, x_3) = (1, 1, 0), (1, 1, 1)$

Total number = 2

- d. Find out all input vectors that can test signal a stuck-at-0 fault. List your results as a table and report their total number.

ANS:

input vector $(x_1, x_2, x_3) = (0, 0, 1), (0, 1, 0), (0, 1, 1), (1, 0, 1)$

Total number = 4

```
All input vectors that can test signal 'a' stuck-at-0 fault
x1 = 0 x2 = 0 x3 = 0 a = 1 b = 1 z = 0 fault_a = 0
x1 = 0 x2 = 0 x3 = 1 a = 1 b = 0 z = 0 fault_a = 1 This input vector can test
x1 = 0 x2 = 1 x3 = 0 a = 1 b = 0 z = 0 fault_a = 1 This input vector can test
x1 = 0 x2 = 1 x3 = 1 a = 1 b = 0 z = 0 fault_a = 1 This input vector can test
x1 = 1 x2 = 0 x3 = 0 a = 1 b = 1 z = 0 fault_a = 0
x1 = 1 x2 = 0 x3 = 1 a = 1 b = 0 z = 0 fault_a = 1 This input vector can test
x1 = 1 x2 = 1 x3 = 0 a = 0 b = 0 z = 1 fault_a = 1
x1 = 1 x2 = 1 x3 = 1 a = 0 b = 0 z = 1 fault_a = 1
Total number of test vectors = 4
```

- e. Try to reason if there is any input vector that can test an “AND-bridging fault” occurring between signals a and signal b? If yes, find out all these test vectors as a table and report their total number

ANS:

Yes, input vector $(x_1, x_2, x_3) = (0, 0, 1), (0, 1, 0), (0, 1, 1), (1, 0, 1)$

Total number = 4

```
AND-bridging fault occurring between signals a and signal b
x1 = 0 x2 = 0 x3 = 0 a = 1 b = 1 z = 0 fault z = 0
x1 = 0 x2 = 0 x3 = 1 a = 1 b = 0 z = 0 fault z = 1 This input vector can test
x1 = 0 x2 = 1 x3 = 0 a = 1 b = 0 z = 0 fault z = 1 This input vector can test
x1 = 0 x2 = 1 x3 = 1 a = 1 b = 0 z = 0 fault z = 1 This input vector can test
x1 = 1 x2 = 0 x3 = 0 a = 1 b = 1 z = 0 fault z = 0
x1 = 1 x2 = 0 x3 = 1 a = 1 b = 0 z = 0 fault z = 1 This input vector can test
x1 = 1 x2 = 1 x3 = 0 a = 0 b = 0 z = 1 fault z = 1
x1 = 1 x2 = 1 x3 = 1 a = 0 b = 0 z = 1 fault z = 1
Total number of test vectors = 4
```

- f. Try to reason if there is any input vector that can test an “OR-bridging fault” occurring between signals a and signal b? If yes, find out all these test vectors as a table and report their total number.

ANS:

No, Total number = 0

```
OR-bridging fault occurring between signals a and signal b
x1 = 0 x2 = 0 x3 = 0 a = 1 b = 1 z = 0 fault z = 0
x1 = 0 x2 = 0 x3 = 1 a = 1 b = 0 z = 0 fault z = 0
x1 = 0 x2 = 1 x3 = 0 a = 1 b = 0 z = 0 fault z = 0
x1 = 0 x2 = 1 x3 = 1 a = 1 b = 0 z = 0 fault z = 0
x1 = 1 x2 = 0 x3 = 0 a = 1 b = 1 z = 0 fault z = 0
x1 = 1 x2 = 0 x3 = 1 a = 1 b = 0 z = 0 fault z = 0
x1 = 1 x2 = 1 x3 = 0 a = 0 b = 0 z = 1 fault z = 1
x1 = 1 x2 = 1 x3 = 1 a = 0 b = 0 z = 1 fault z = 1
Total number of test vectors = 0
```